

ESE-2005 Lab 6 Single-Cycle Micro-architecture

Exercise

1. Review our slides carefully. Suppose that one of the following control signals in the single-cycle **ARM** processor has a stuck-at-0 fault, meaning that the signal is always 0, regardless of its intended value. What types of instruction would malfunction? Why?
 - a) PCSrc
 - b) $ALUControl_{1:0}$
 - c) MemW
 - d) ALUSrc